

Basic Electronics - Formula Sheet

Basic Electronics Formula Sheet

Ohm's Law

$$V = I * R$$

Power

$$P = V * I = I^2 * R = V^2 / R$$

Diodes

- **Forward Bias**: Current flows easily.
- **Reverse Bias**: Minimal current flows.
- **Shockley Equation**: $I = I_s * (e^{(V/nV_t)} - 1)$

Transistors (BJT)

- $I_E = I_B + I_C$
- Beta (Current Gain) = I_C / I_B
- Alpha = I_C / I_E

Op-Amps

- **Inverting Amplifier**: $V_{out} = -(R_f/R_{in}) * V_{in}$
- **Non-Inverting Amplifier**: $V_{out} = (1 + R_f/R_{in}) * V_{in}$